



MINI – PROJECT REPORT

SUBMITTED BY :

EDEN JOSEPH 221682

MUHAMMAD ABDULLAH KHAN 221748

EIHAAB 221751

SUBMITTED TO :

ENGR. MUZZAMIL GHAFAR

DATE : 14/03/2023

WORKING PRINCIPLE

The objective is to make a dc power supply that takes 220V AC input, and converts that 220V to 12-15V AC using a step down transformer.

After the current has been stepped down, it goes through a bridge rectifier that converts it to DC Current which is about 12 – 13 Volts


Then we have used to IC's LM7805 that converts the current to constant 5V and LM317 that also us to connect a potentiometer so that we can vary the voltage by varying resistance

The List Of Components Is Provided Below :


| | | | | |
|-----------------------|--------------|------------|------------|-----------|
| 0 Modules | | | | |
| Quantity | References | Value | Stock Code | Unit Cost |
| Sub-totals: | | | | |
| 5 Capacitors | | | | |
| Quantity | References | Value | Stock Code | Unit Cost |
| 3 | C1-C2, C4 | 100uF | | |
| 1 | C3 | 10nF | | |
| 1 | C5 | 100pF | | |
| Sub-totals: | | | | Rs0.00 |
| 3 Resistors | | | | |
| Quantity | References | Value | Stock Code | Unit Cost |
| 1 | R1 | 220 | | |
| 1 | R2 | 470 | | |
| 1 | R3 | 1k | | |
| Sub-totals: | | | | Rs0.00 |
| 2 Integrated Circuits | | | | |
| Quantity | References | Value | Stock Code | Unit Cost |
| 1 | U1 | 7805 | | |
| 1 | U2 | LM317T | | |
| Sub-totals: | | | | Rs0.00 |
| 0 Transistors | | | | |
| Quantity | References | Value | Stock Code | Unit Cost |
| Sub-totals: | | | | |
| 6 Diodes | | | | |
| Quantity | References | Value | Stock Code | Unit Cost |
| 4 | D1-D4 | 1N4007 | | |
| 1 | D5 | LED-PURPLE | | |
| 1 | D6 | LED-YELLOW | | |
| Sub-totals: | | | | Rs0.00 |
| 7 Miscellaneous | | | | |
| Quantity | References | Value | Stock Code | Unit Cost |
| 1 | FU1 | 1A | | |
| 2 | INPUT,OUTPUT | TBLOCK-I2 | | |
| 1 | J1 | CONN-SIL3 | | |
| 1 | POT | 5k | | |
| 1 | TR1 | TRAN-2P2S | | |
| 1 | V1 | VSINE | | |
| Sub-totals: | | | | Rs0.00 |

LAYOUT ON PROTEUS :




At 100 Resistance Using Potentiometer

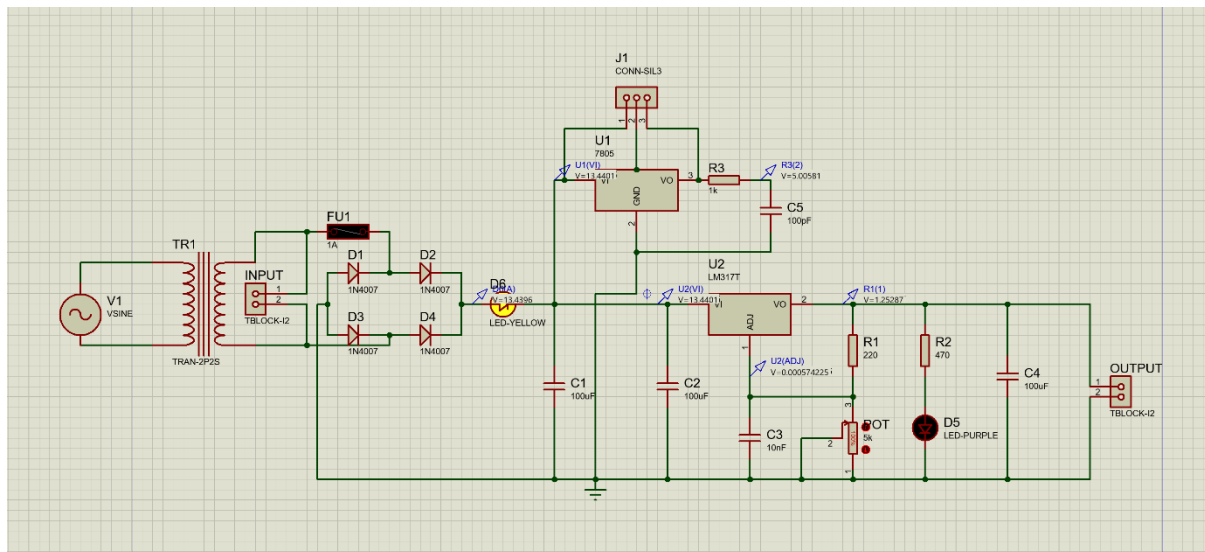



At 0 Resistance Using Potentiometer

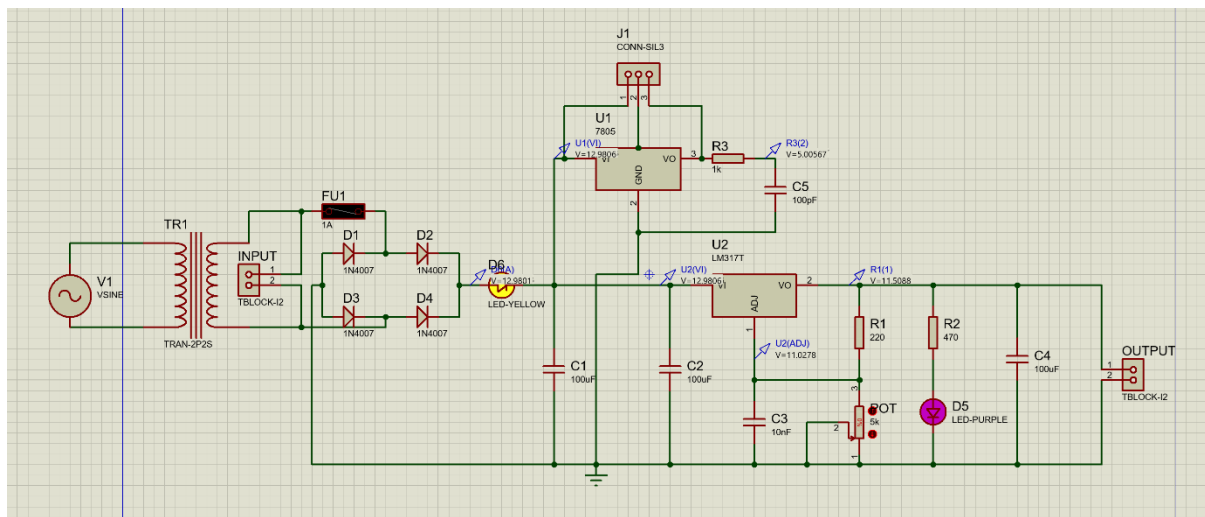



PCB LAYOUT :

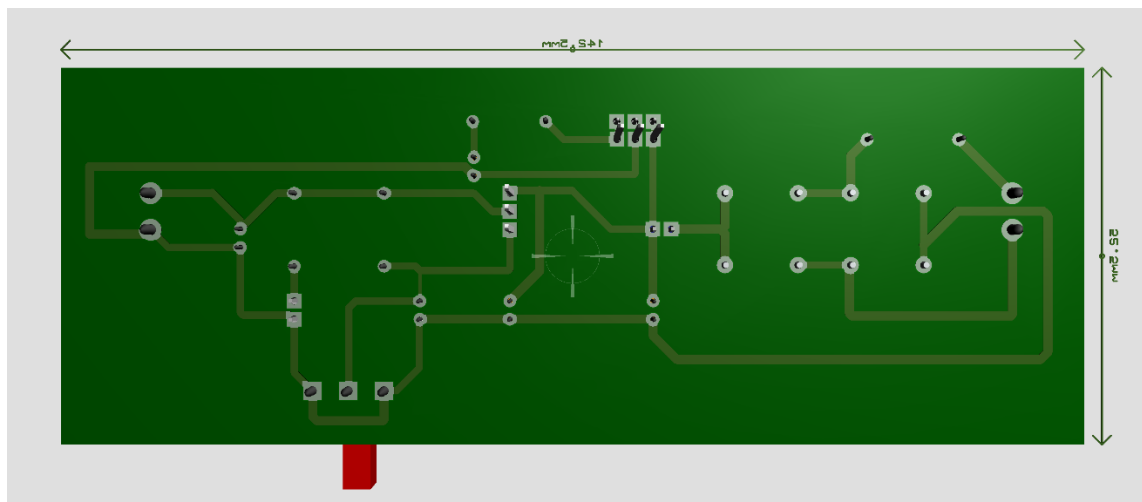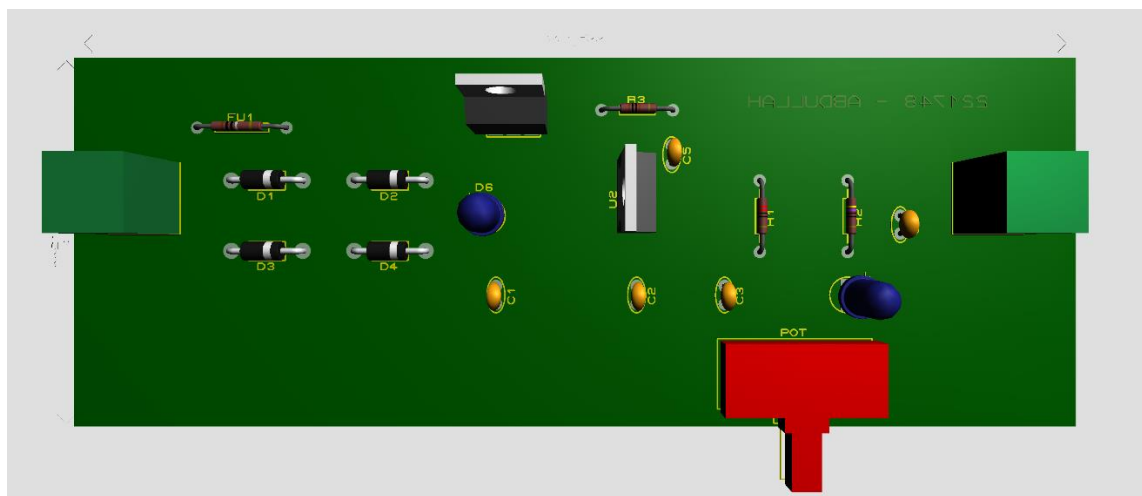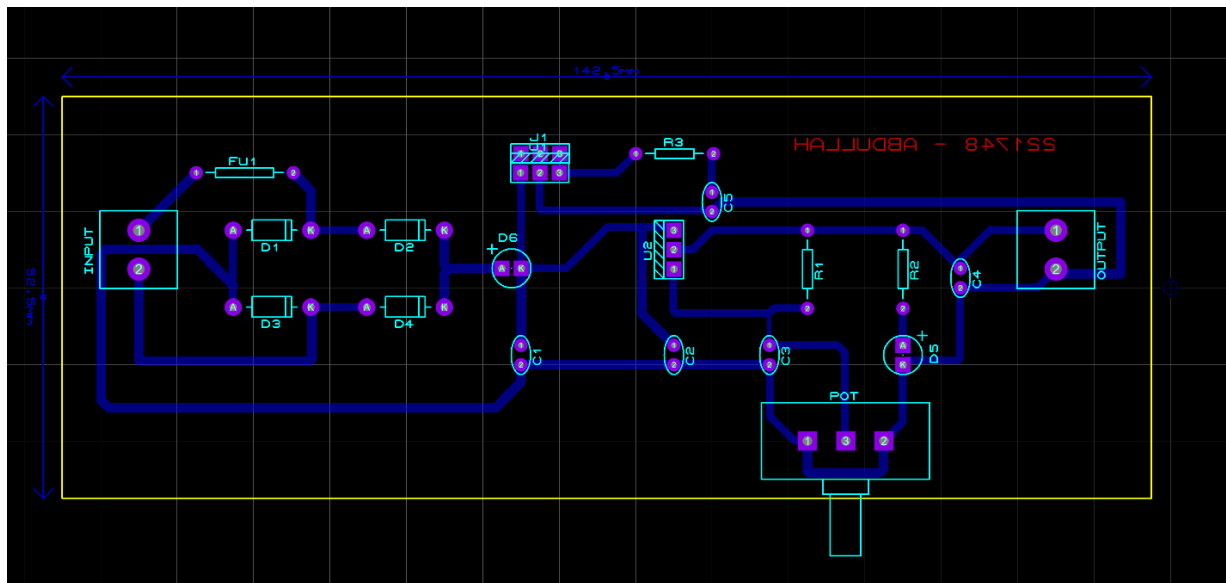


BREADBOARD TESTING.mp4

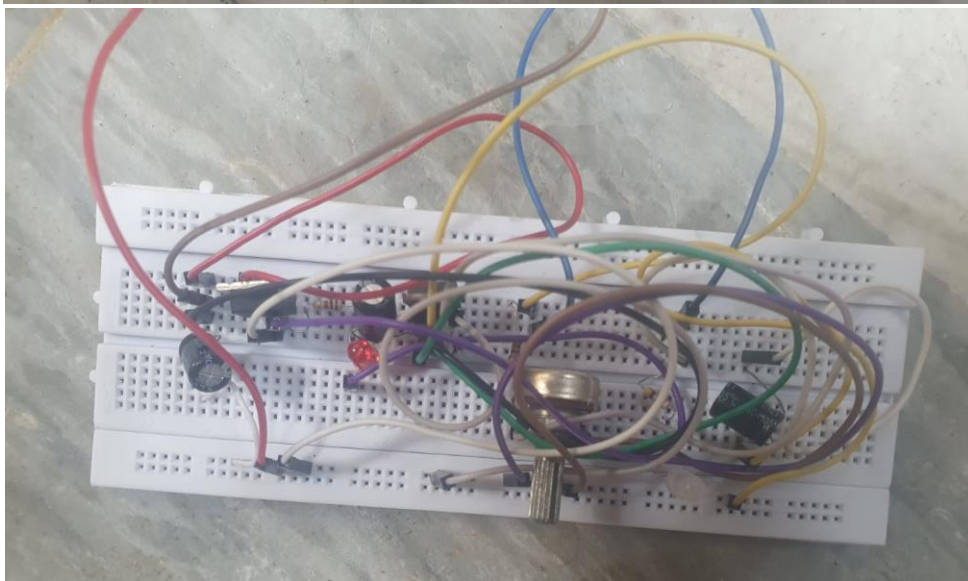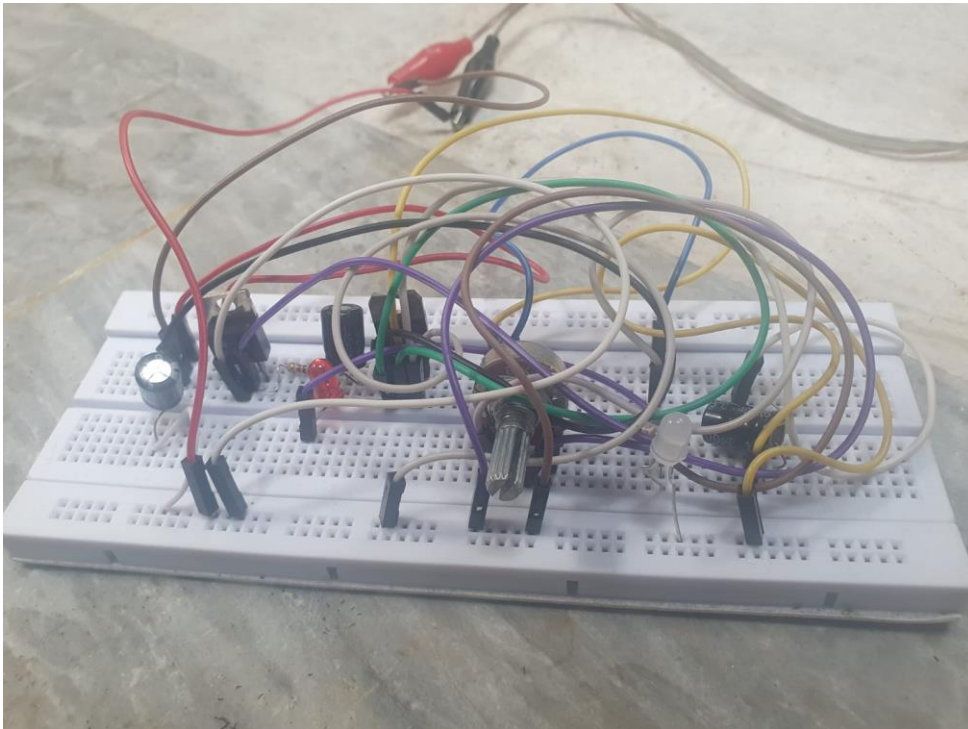

PCB IMAGES

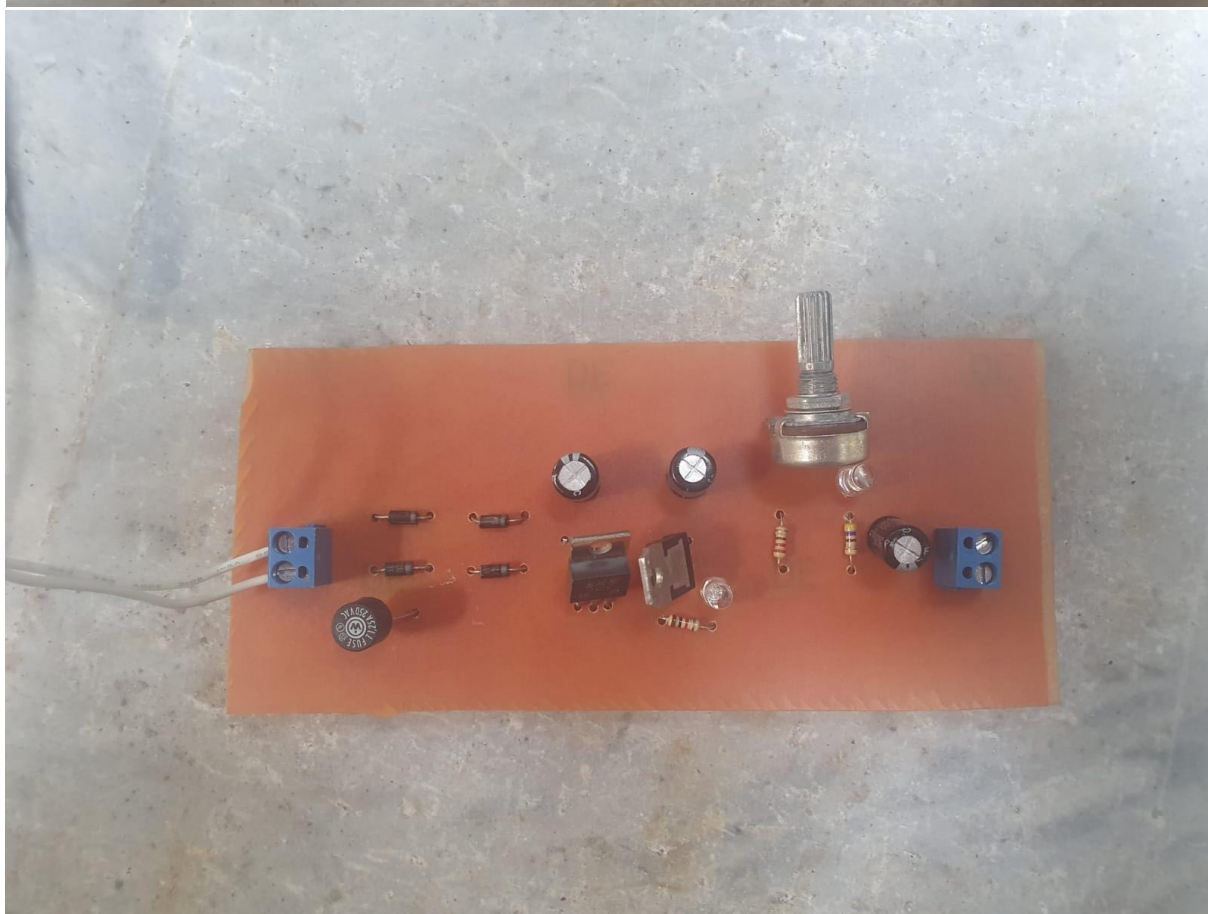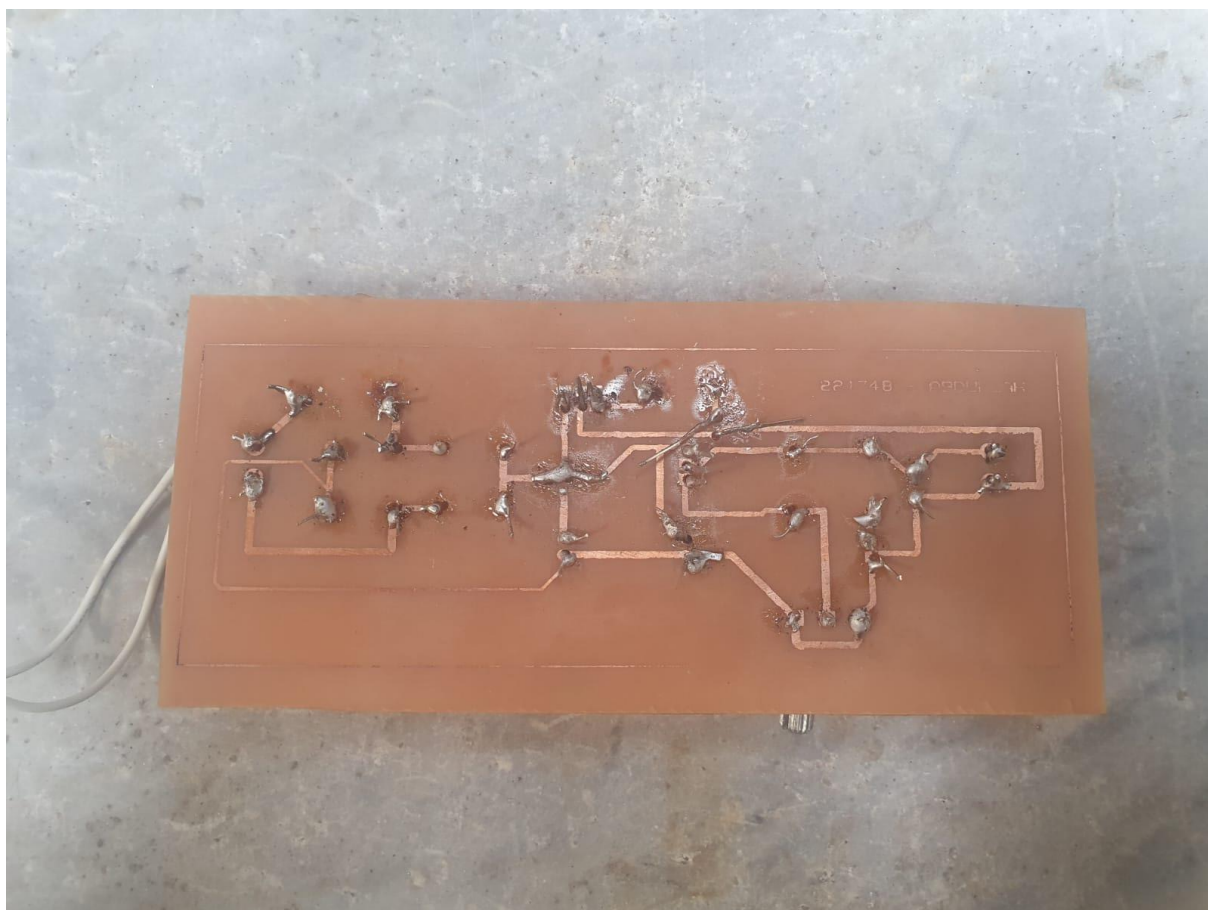

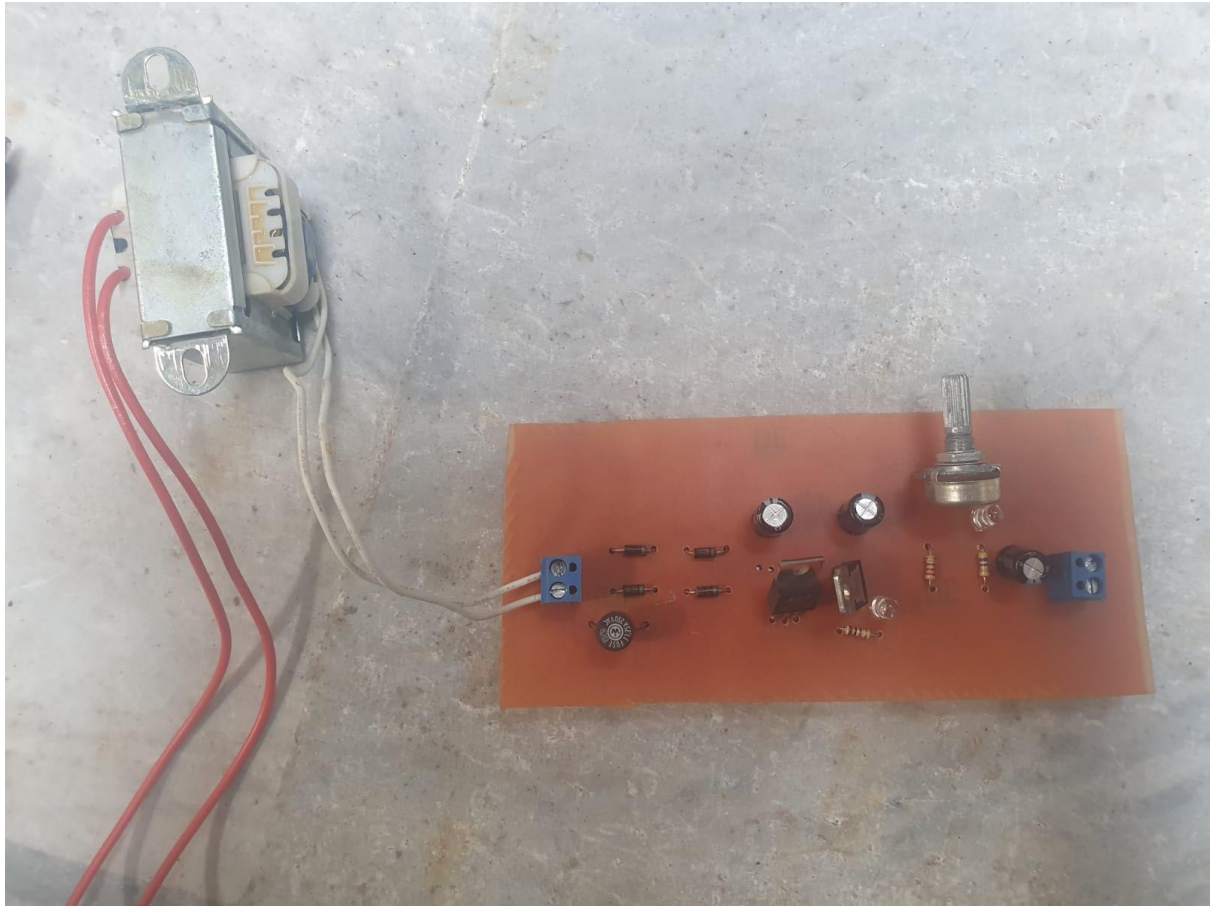

END OF REPORT
